

COMPUTER SYSTEMS 1

DR. JOHN T. O'DONNELL

*Joao Almeida-Domingues**

University of Glasgow

January 7th, 2019 – May 24th, 2019

CONTENTS

1	Analogue and Digital Representation	2
1.1	Computer Systems	2
1.2	Data Representation	2
2	Number Systems	3
2.1	Conversion	3
2.2	Operations	4
3	Logic Gates	6
3.1	Combinational Circuits	7
4	Boolean Algebra & Arithmetics	9
4.1	Laws	9
4.2	Arithmetic: Adding 2 Integers	10
5	Synchronous Circuits	10
6	Register Transfer Machine	12
6.1	Register File	12
6.2	RTM Circuit	13

*2334590D@student.gla.ac.uk

1 ANALOGUE AND DIGITAL REPRESENTATION

1.1 Computer Systems

Lecture 1
January 8th, 2019

1.1 definition. Digital Circuits Electronic systems which use very large numbers of only a few types of components, which when connected the right way create incredibly complex, useful behaviour

1.2 definition. Machine Language Programming language executed directly by the computer hardware, which serves as the interface between low-level circuits and high-level software. Therefore, it is simple enough so that a digital circuit can be designed to execute it, yet also powerful enough that high-level languages can be converted into it

1.2 Data Representation

There are several digital data types which need somehow be represented in hardware. This is done by encoding electrical signals (voltage). It is by manipulating these voltages in the hardware that computations are able to be performed. There are 2 ways of achieving this:

1. Analogue

1.3 definition. The variables in the calculation are *analogue* to the physical signals being measured (e.g. $1 \iff 3\text{v}$)

There are some advantages to this method, such as fast calculation of differential equations. Unfortunately, it also has significant drawbacks: limited precision; errors accumulate; difficult to represent non-numerical data

2. Digital

1.4 definition. As indicated by the root of the word, it makes use of digits. It is by counting that calculations can be performed.

This addresses some of the drawbacks of analogue computing. For example, one can always add more digits when higher precision is required; Handles noise and errors better; Easy representation of most data types

1.5 definition. Bit Unit of information used in digital circuits. It represents either a 0 or a 1

1.6 remark. Different circuits use different voltages, but the more simpler and reliable ones tend to use just two clearly distinct voltages to represent each value (0,1)

1.7 definition. Flip Flop The simplest circuit with memory. Basic element of computer memory

1.8 definition. Byte 8 bits

Note that just like in any other positional number system, the number of possible representations grows exponentially with the number of digits added. In the binary system we only have 0, 1. But by using basic knowledge of combinatorics, one observes that for every new position n the number of possible orderings doubles. It follows, for example, that for an 8 bit binary number one can represent up to $2^8 = 256$ different values ($0 \rightarrow 255$). In general, for a k bit number:

$$2^k \text{ possible values. From } 0 \text{ until } 2^k - 1$$

1.9 notation. By convention, 4 bits are separated by a space for readability

0000 0000

1.10 definition. Word For convenience, for larger numbers of bits, the term *word* is used. The specific number of bits which a word represent changes. For this class: 16, 32, 64 = short w., w., long w.

Lecture 2
January 10th, 2019

2 NUMBER SYSTEMS

2.1 Conversion

Conversions between different bases are easily achieved, by keeping in mind the simple fact that each position is able to represent a minimum value, and a maximum value, every time that value is exceeded, we need another "slot" to reset the counting with the "symbols" (i.e the digits) available in that system. To make it clear, let's first look at the decimal system, as first learned in primary school. 19_{10} can be thought of $10 + 9$, which in turn can be thought of 9 single units + 1 single "10" unit. Since 9 is the highest "unit symbol" available in the decimal number system we need another slot "the tenths". Transitioning from 9 to "10". Note how the "counter" was reset to 0 and we now start counting again from 1, but in the tenths and in the units slot. We don't need to add another slot until all digits, in all possible combinations, have been used.

Similarly, binary/base 2, simply means that for every "slot" we have only two symbols at our disposal, 0 and 1. And instead of thinking of the slots as 10^{th} , 100^{th} , ... we think in terms of powers of 2.

$$\left| \begin{array}{c|c|c|c} 128 & 64 & 32 & 16 \\ 2^7 & 2^6 & 2^5 & 2^4 \\ \hline 0 & 0 & 0 & 0 \end{array} \right| \left| \begin{array}{c|c|c|c} 8 & 4 & 2 & 1 \\ 2^3 & 2^2 & 2^1 & 2^0 \\ \hline 0 & 1 & 1 & 1 \end{array} \right| = 4 + 2 + 1 = 7_{10}$$

From decimal to binary the process is similar, but in reverse. If a primary school child was given a decimal table, and was asked to fill it with 150, she would obviously not start by the units and start incrementing 1-by-1. She would notice that she'll need at least the 1 unit of "100" (10^3) and immediately put a 1 in the 3rd slot, and then notice that she'll need 5 "10s" and so on. This is trivial, and similarly trivial it is for base 2. Say you're given 74_{10} . What is the highest slot you can immediately fill? Well, 128 it's too high, the one before it is $64 = 2^7$ (position 7). That works, but it still leaves us with 10 units to be represented. Repeating the process, we see that we'll need an $8 = 2^3$ (position 3) and a 2 (position 2) until all units have been distributed amongst the "slots". Giving us:

0100 1010

This process is less straightforward for other bases, simply because we're used to think in base10. But the method is similar for all. Another useful base is **base 16**, where we use the letters A - F to represent the numbers from $10 \rightarrow 15$. This has the obvious advantage of reducing the number of "symbols"/characters needed for representing a binary number. For example: an 8 bit number can be easily represented by just 2 characters, with plenty leftover, since $16^2 = 256$ possible values.

2.1 notation. For this class "\$" is used to represent hexadecimal numbers

The simplest way to convert from Binary to Hex is simply to note that, we need 4 bits to represent 1 hexadecimal bit in its entirety (i.e. 0 - F). Hence we split the number into 4 bit chunks and convert them into the corresponding hex character. Such that the first 4 bits correspond to the hex uni bit, the next 4 bits to the "16^{ths}", etc.

0	1	0	0	1	0	1	0
4				A			

The reverse is done in the same way as in the decimal above, but again working only in 4 bit chunks

2.2 remark. Note however that it is always more natural to filter through decimal instead of thinking " $2^4 - 1 = F$ "

2.2 Operations

Multiplication and Addition are performed much like in the same way we perform operations in decimal, again keeping in mind the digits available to work within each system, every time we exceed the limit we must carry onto the next.

Subtraction can be seen as a special case of addition with negative numbers, i.e. $3 - 2 = 3 + (-2)$. Binary numbers cannot represent negative numbers however, so we use **2's complement**. A 2c number is negative if its leftmost digit is 1

2.3 remark. Note that this does not affect the number of possible values that can still be represented, but it reduces the possible positive number representations in half, since for every positive number there will be a corresponding negative.

The general conversion method is straight forward:

1. Invert the bits
2. Add 1

It can be useful to think of the rightmost digit of an n bit 2c number as always representing the sum of the highest possible negative number ($-2^{(n-1)}$) with an $n - 1$ bits positive number. The n^{th} bit is just the sign bit

2.4 remark. Note that, by adding all the positives we'll get 0, in which case the sign bit is turned off. We can think of 0 as belonging to the positives in this case, since it has the sign bit off. But when not considering it, even though we can represent $2^{(n-1)}$ negative numbers we can only represent $2^{(n-1)} - 1$ positive ones. Since the " n^{th} " would in effect be 0.

2.5 example.
$$\begin{array}{c|c|c|c} 1 & 0 & 1 & 0 \\ -8 & +0 & +2 & +0 \end{array} = -6$$

Since it is a 2c number we know we can represent up to $2^3 = 8$ different values in each "direction" (considering 0 a positive number). So we have -8 and then we need to find out the 3bit binary. ($0 \cdot 2^0 + 1 \cdot 2^1 + 0 \cdot 2^2 = 2$). And then add them

It is clear from the example above how subtraction and division can then be performed just like addition

except from the lowest possible negative, which positive counterpart will always need an extra bit, since we're counting from 0

3 LOGIC GATES

Lecture 3
January 15th, 2019


3.1 definition. Logic Gate A physical, basic component, which takes 1+ input(s) and performs a boolean function (i.e the result is either T/F)

1. Inverter

3.2 definition. Takes an input and returns its opposite

3.3 notation. `inv`

*alternatively \bar{p}

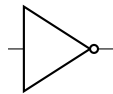


p	$\neg p^*$
1	0
0	1

2. 2-Input AND

3.4 definition. Returns true *iff* the two inputs are true

the 2 used in the gates' names just means that 2 inputs are passed

3.5 notation. `and2`

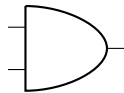

p	q	$p \wedge q$
1	0	0
1	1	1
0	0	0
0	1	0


3.6 remark. Note that for a n input truth-table, there are 2^n possible input combos

3.7 remark. An easy way to construct truth tables is to start half(1)-half(0), then $\frac{1}{4}$, $\frac{1}{8}$, \dots . So for a 3 input table, one first put 4 1s, 4 0s. Then, half of that, i.e. 2 1s 2 0s $2\times$, and finally 1, 0, $8\times$

3. 2-input OR

3.8 definition. Returns true if any one of the two inputs are true, or if both are true

3.9 notation. `or2`

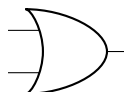


p	q	$p \vee q$
1	0	1
1	1	1
0	0	0
0	1	1

4. 2-input XOR

3.10 definition. Returns true *iff* one of the two inputs is true

3.11 notation. xor2

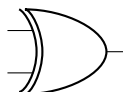

p	q	$p \vee * q$
1	0	1
1	1	0
0	0	0
0	1	1

* \oplus

3.1 Combinational Circuits

3.12 definition. Combinational Circuits Their output depends only on their current input. There's no feedback loop, or "memory" state

For complex circuits it is hard to keep track of every input and output by just connecting single logic gates. It is useful to create *black box circuits* to abstract some of the complexity out. These components, regardless of what logic gates are used to built them*, always perform the same operation (e.g. choosing between two inputs).


*hence the name black box

1. Multiplexer

3.13 notation. mux1

3.14 definition. Hardware equivalent of the "if-then-else" statement. Chooses between 2 values (x, y) given a third (c). If c y , else x

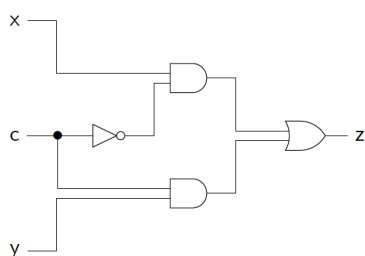3.15 remark. Every decision a computer makes comes down to a multiplexer




c	x	y	z
1	1	1	1
1	1	0	0
1	0	1	1
1	0	0	0
0	1	1	1
0	1	0	1
0	0	1	0
0	0	0	0

2. Demultiplexer

3.16 definition. The opposite of a multiplexer, it takes a single input converts it into several outputs. It is used to select where to send the input data

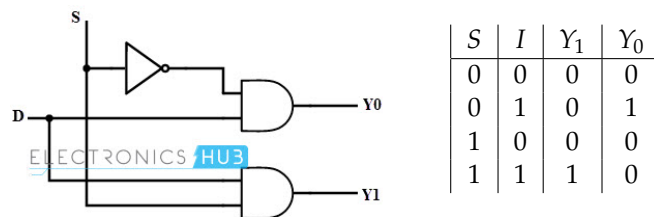
3.17 remark. For 2^n possible outputs, n selection signals/lines are required (i.e. 1-to-2 dmux requires 1 control signal)



3. Half-Adder

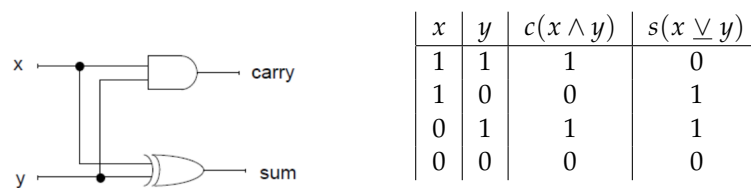3.18 definition. Adds two bits using a 2-bit (carry,sum) representation.


Note that there's only a carry if both inputs are 1, hence we represent this by an and2 gate, while the sum can be represented by an xor2



4. Full-Adder

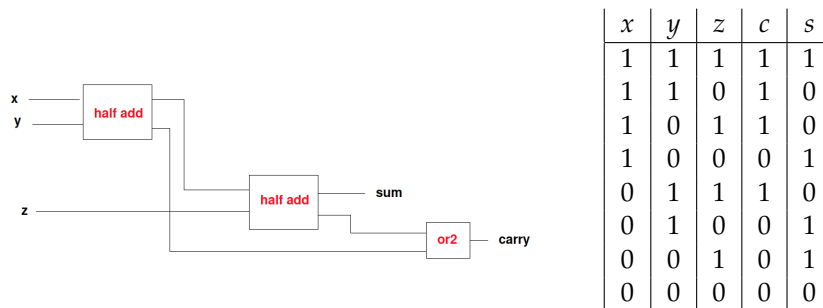3.19 definition. Adds three bits (inputs + carry) using a 2-bit (carry,sum) representation.

Note that there's only a carry when 2+ inputs are 1, and there's only a sum iff there are an odd number of inputs equal to 1



4 BOOLEAN ALGEBRA & ARITHMETICS

4.1 Laws

Lecture 4
January 17th, 2019

4.1 definition. Idempotence operation that can be applied several times without changing the result

$$x \vee x = x \quad x \wedge x = x$$

4.2 definition. Commutative operations can be performed in any order

$$x \vee y = y \vee x \quad x \wedge y = y \wedge x$$

4.3 definition. Associative the order in which the operations are performed does not matter as long as the sequence of the operands is not changed

$$x \vee (y \vee z) = (x \vee y) \vee z$$

$$x \wedge (y \wedge z) = (x \wedge y) \wedge z$$

Proof.

x	y	z	$y \vee z$	$x \vee y$	$x \vee (y \vee z)$	$(x \vee y) \vee z$
1	1	1	1	1	1	1
1	1	0	1	1	1	1
1	0	1	1	1	1	1
1	0	0	0	1	1	1
0	1	1	1	1	1	1
0	1	0	1	1	1	1
0	0	1	1	0	1	1
0	0	0	0	0	0	0

QED

4.4 definition. Distributive & Absorption

$$x \wedge (y \vee z) = (x \wedge y) \vee (x \wedge z)$$

$$x \vee (y \wedge z) = (x \vee y) \wedge (x \vee z)$$

5. SYNCHRONOUS CIRCUITS


$$x \wedge (x \vee y) = x$$

$$x \vee (x \wedge y) = x$$

4.5 remark. Useful for prove of correctness

4.2 Arithmetic: Adding 2 Integers

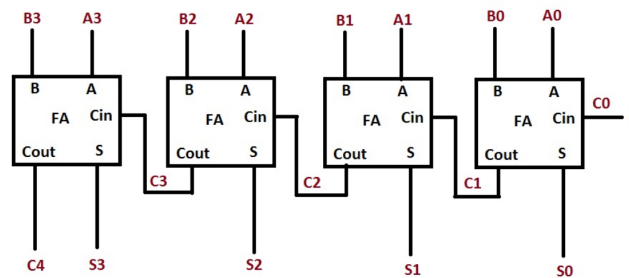4.6 definition. **4-bit Ripple Carry Adder** Uses 4 full adders to add two 4-bit numbers



4.7 remark. Note how the carry from each previous operation is passed onto the next, just like how one does addition manually

4.8 remark. Subtraction can be done much in the same way, by first applying 2's c to one of the inputs

5 SYNCHRONOUS CIRCUITS


Given that logic gates are physical devices, there is a time delay between an input change and the new output. This makes the circuit stop obeying the boolean laws

5.1 remark. the clock running faster than it should may lead to invalid outputs, but if it is running slower it simply leads to loss of computational performance/speed

5.2 remark. Even though the time delay for a gate is marginal, for a whole circuit the delays add up

5.3 definition. **Gate Delay** Time taken for a gate to respond to a change of input with the correct output

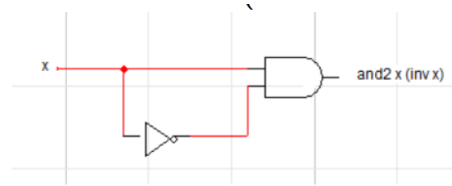5.4 example. The expected output of the following circuit would be 0, however when changing from, 1 to 0, the delay of the inv gate will cause both inputs of the and gate to be 1, which in turn will erroneously output a 1



5.5 definition. State The stored contents of the memory elements of a circuit, at a given point in time, is collectively referred to as the circuit's state and contains all the information about the past to which the circuit has access

5.6 definition. Delay Flip Flop (dff) component which endows a circuit with state. It has 2 inputs (saved value, clock tick) and 1 output (state value)

Every time the dff receives a clock signal, it updates its state value. Since the physical components deal with analogue signals, the *clock tick* can not be represented discretely. The workaround is to have the dff treat the voltage spike as the tick

There is only one clock signal for all flip flops, hence they are all updated simultaneously

5.7 remark. The output of a dff is independent of its input



5.8 definition. Synchronous Circuit

1. Every flip flop must be directly connected to a global clock
2. No logical functions can be applied to the clock signal
3. Every clock tick must reach all flip flops simultaneously
4. Every feedback loop must pass through a flip flop
5. The inputs to the circuit remain stable throughout clock cycles


The cycle must be long enough to allow for all signals to become valid

At every clock tick the dff state gets updated, in order to store its state for longer we can use a register (reg1). If the control input is 1, then the value from the dff is loaded into the reg1 otherwise it remains the same. The conditional is implemented by an mux1

5.9 definition. Register Allows the bit to be recorded between cycles, until a new value is loaded. It takes 2 inputs (ld =1,0 and the value bit) and it outputs the state bit

$$\text{dff_input} = \text{mux1 } \text{ld} \text{ old.state } x$$

6. REGISTER TRANSFER MACHINE

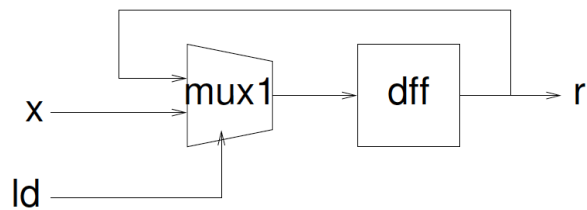

The register can be simulated by way of a simulation table:

Cycle	Inputs		State	Internal
	ld	x	r	dff_input
0	1	1	?	1
1	1	0	1	0
2	0	1	0	0
3	1	1	0	1

6 REGISTER TRANSFER MACHINE

Lecture 5
January 25th, 2019

The purpose of an RTM is to use the memory provided by the registers we've learned about in the last lecture to allow simple assignment statements to memory and arithmetic operations to be carried out. To be able to achieve this in a digital circuit, we'll need (1) simple statements (2) A small number of types of statement with a fixed form

6.1 definition. Opcode portion of a machine language instruction that specifies the operation to be performed

6.2 definition. Instruction a group of several bits in a computer program that contains an opcode and usually one or more memory addresses

6.3 notation. Assignment $x := y$

6.4 example. Performing an assignment operation, between the value 2 and the Register 1:


$R1 := 2$

6.1 Register File

6.5 definition. Register File Array of registers (5.9)

The register file circuit enables the user to:

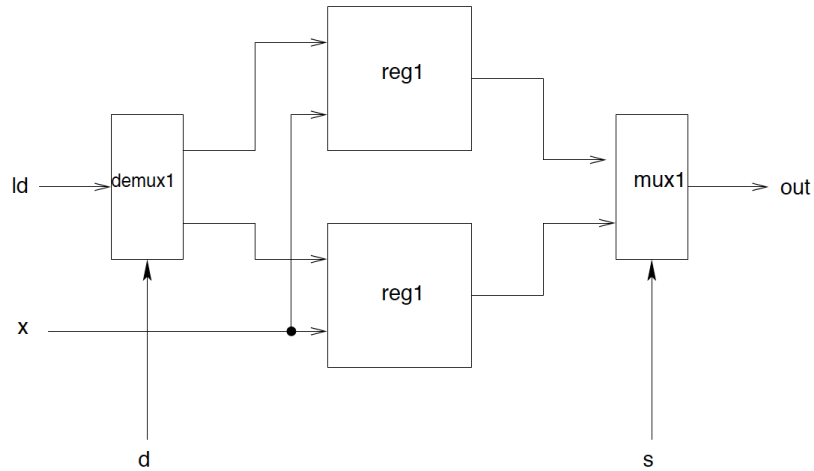1. Specify, address and read out a specific register
2. Specify and load a value into a new address



Inner Workings

- The operation to be performed is controlled by *control signals*. These include:
 - the “on”/“off” signal or the “load” signal ld
 - the memory addresses to the individual registers d , s
 - “read”/“write”
- The input passed onto the circuit x is loaded into one of the registers **only** when a clock tick occurs **and** if $ld = 1$.
- During the cycle select operations may occur, and in the end data is output from a specific register using a memory address passed as another control signal s


6.6 remark. Note that only the register at address d will be modified, since the demultiplexer (3.16) will make sure that any other register will have a load control of 0

6.7 remark. Note also that since a $dmux$ (3.16) is able to generate 2^n outputs from n inputs, it follows that for controlling a k bit register only \sqrt{k} address bits are required

6.8 remark. When more than one address needs to be read out, we can pass more source addresses (s_1 s_2 s_3) into the multiplexer

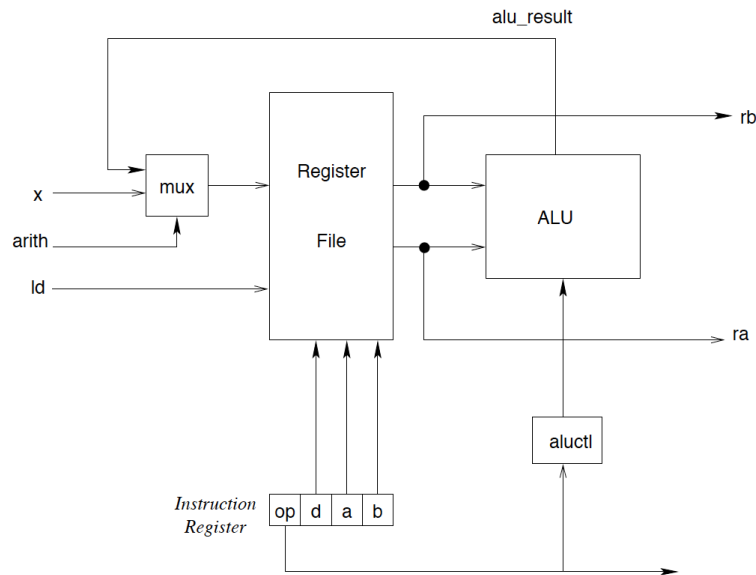6.2 RTM Circuit

Note that the register file allow us to update and read values from inputs, but our intention is to also be able to perform simple arithmetic operations on the values in the registers. This can be done by connecting an adder and a register file in a feedback loop, i.e. the n outputs of the register file, become the n inputs of the adder



Inner Workings

- A multiplexer is added, which allow the user to decide wether to pass onto the register a new value or to pass the result from the adder (hence the feedback)
- If the select signal is on $arith = 1$, then the file register circuit loads into the register $[d]$ the result of the adder in the way describe above
- Otherwise, it simply loads the new external output

```

if ld
  then if arith
    then reg[d] := reg[sa] + reg[sb]
    else reg[d] := x

```

So now we have a 3rd useful feature provided by the RTM (on top of the 2 previously seen provided by the register), the possibility of adding two numbers *in memory*. So the following is now possible:

1. Assign an external input to a register $R[address] = constant$
2. Adding (or subtracting) two values in memory $R[a] = R[b] + R[c]^*$

the two values being added can be from the same register $R[a] = R[b] + R[b]$

6.9 remark. Note however that the following is not possible *within one cycle* $R[a] = c + R[b]$, since c is not in memory

REFERENCES

wikipedia

URL: <https://en.wikipedia.org/wiki/Wikipedia>.

Basic Electronics Tutorials and Revision

basic'electronics

Basic Electronics Tutorials and Revision. URL: <https://www.electronics-tutorials.ws/>.

Petzold: Code: the hidden language of computer hardware and software
petzold'2001

Charles Petzold. *Code: the hidden language of computer hardware and software*. Microsoft Press, 2001.

Velleman: How to prove it: a structured approach

velleman'2009

Daniel J. Velleman. *How to prove it: a structured approach*. Cambridge University Press, 2009.